
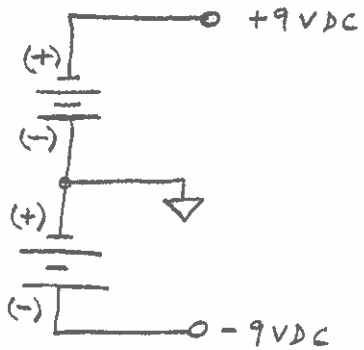


POWER SUPPLY FOR OP-AMPS:

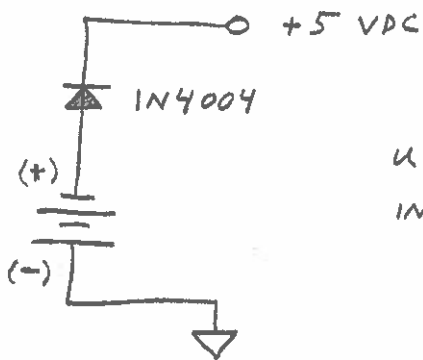

USE TWO 9 VOLT TRANSISTOR
RADIO BATTERIES IN SERIES.

POWER SUPPLY FOR DIGITAL LOGIC:



USE A 6 VOLT LANTERN BATTERY
IN SERIES WITH A DIODE.