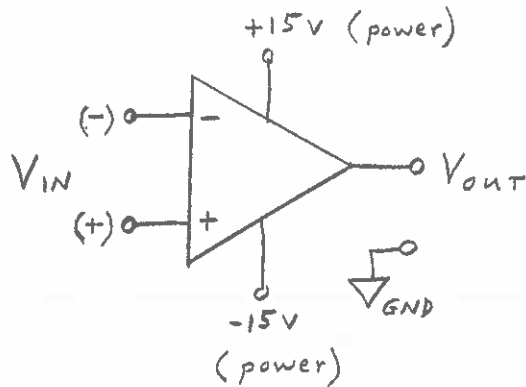


OPERATIONAL AMPLIFIER (OP-AMP)



Input and output voltages are in the range of $+10\text{v}$ to -10v with respect to ground.

Output voltage V_{out} is with respect to ground.

Input voltage is $V_{IN}(+)$ with respect to $V_{IN}(-)$.

Either input can be connected to gnd or to any other voltage between $+10\text{v}$ and -10v .

For Design Purposes:

Assume input impedance = ∞ infinity (It's typically = 10Meg ohm)
Therefore, no current flows into inputs.

Assume gain, $V_{out}/V_{IN} = \infty$ infinity (typically = 1 million)

If $V_{IN}(+) > V_{IN}(-)$, then V_{out} saturates at $+10\text{v}$.

If $V_{IN}(+) < V_{IN}(-)$, then V_{out} saturates at -10v .

* $\left\{ \begin{array}{l} V_{out} \text{ stays between } \pm 10\text{v} \text{ (normal linear operation)} \\ \text{only when } V_{IN}(+) = V_{IN}(-) . \end{array} \right.$


↪ This last condition is obtained by the clever use of feedback components (resistors and capacitors).

Over-all gain of circuit is controlled by feedback components.

For proper operation, gain should be less than 100,

and resistors should be between 1K ohm and 1Meg ohm .

EXAMPLE #1: Unity Gain Buffer:

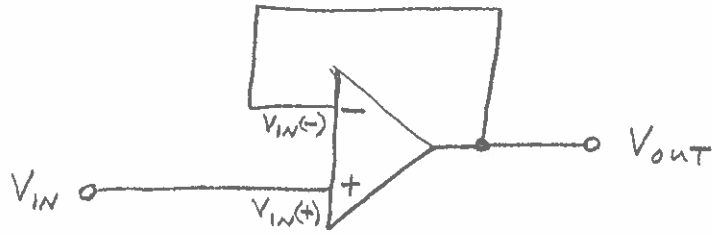


$$\text{Gain} = +1$$

$$V_{\text{OUT}} = V_{\text{IN}}$$

The purpose of this circuit is to monitor a voltage (V_{IN}) from a delicate source without loading it down (without drawing any current) and transferring this voltage to a circuit that draws up to 1 milliamp such as a 1K ohm resistor.

* { To understand intuitively how this circuit works, just think what voltage V_{OUT} has to go to in order to make $V_{\text{IN}}(-) = V_{\text{IN}}(+)$.

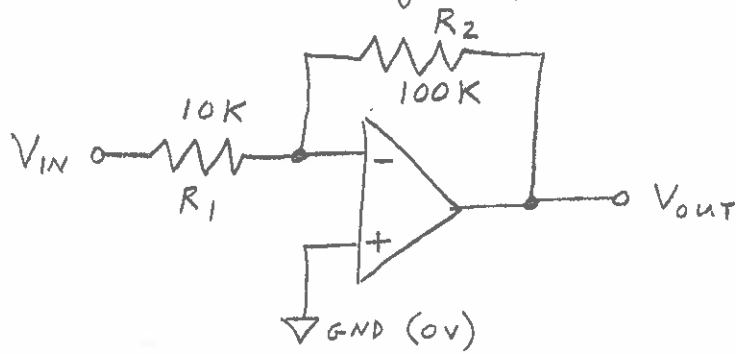EXAMPLE #2: Inverting Amplifier (most common circuit)



$$GAIN = V_{OUT}/V_{IN} = -R_2/R_1 = -10$$

$$V_{OUT} = (-R_2/R_1) * (V_{IN})$$

If +0.5 v is applied at V_{IN} ,

$$\text{then } V_{OUT} = -R_2/R_1 * V_{IN} = -10 V_{IN} = -5V .$$

* { To understand this intuitively, just think what voltage V_{OUT} has to go to in order to make $V_{IN}(-) = V_{IN}(+) = 0V$.

Current through R_1 is $I_1 = V_1/R_1 = 0.5V/10K\Omega = 50\mu\text{Amp}$.

Current through R_2 is I_2 .

$I_2 = I_1$ because I_1 has to go somewhere, and it doesn't go into op-amp because input impedance = ∞ .

Voltage across R_2 is V_2 .

$$V_2 = I_2 * R_2 = 50\mu\text{A} * 100K\Omega = 5V \quad (\text{below } 0V)$$

or $-5V$.